


# Logical Effort

Monday, March 08, 2010  
09:04

TA Stuff

Midterm 3/15/2010 : 7-9PM

→ 1 handwritten cheat sheet

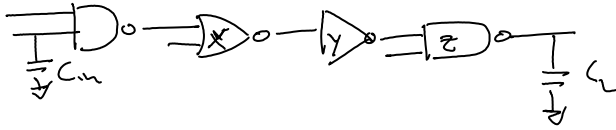

$$D = \sum_{i=1}^N D_i = \sum_{i=1}^N P D_i + \sum_{i=1}^N \underbrace{L E_i F O_i}_{SE_i \text{ (Stage Effort)}}$$

$$\text{Path Effort (PE)} = \prod_{i=1}^N SE_i = \prod_{i=1}^N L E_i \cdot \prod_{i=1}^N F O_i$$

path logical effort
aka path electrical effort

$\frac{C_{out}}{C_{in}}$

Recall that for a chain of buffers,  $f = \sqrt[N]{F}$

$$\Rightarrow SE^* = \sqrt[N]{PE}$$


$$L E_i \cdot F O_i = SE^*$$

$$L E_i \cdot \frac{C_{gate, i+1}}{C_{gate, i}} = SE^*$$

$$C_{gate, i+1} = \frac{SE^*}{L E_i} \cdot C_{gate, i}$$

$$C_{gate, i} = \frac{L E_i}{SE^*} \cdot C_{gate, i+1}$$

Example 1

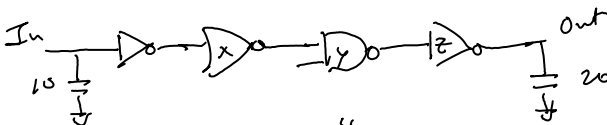

$$PE = \prod_{i=1}^4 SE = \left(1 \cdot \frac{10}{10}\right) \cdot \left(\frac{5}{3} \cdot \frac{4}{4}\right) \cdot \left(\frac{4}{3} \cdot \frac{2}{4}\right) \cdot \left(1 \cdot \frac{20}{20}\right)$$

$$= \frac{40}{9}$$

$$N=4$$

$$\Rightarrow SE^* = \sqrt[4]{\frac{40}{9}} \approx 1.45$$

$$LE_{in} \cdot F_{out} = 1.45$$

$$1 \cdot \frac{x}{18} = 1.45 \Rightarrow x = 26.1$$

$$LE_{in} \cdot F_{out} = 1.45$$


$$\frac{5}{2} \cdot \frac{y}{14.5} = 1.45 \Rightarrow y = 12.7$$

$$LE_{in} \cdot F_{out} = 1.45$$

$$\frac{4}{3} \cdot \frac{z}{12.7} = 1.45 \Rightarrow z = 13.8$$

$$D = N \cdot SE^* + \sum_{i=1}^N PD_i$$

## Branching Effort

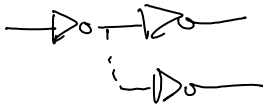


$$b_i = \frac{C_{on-path} - C_{off-path}}{C_{on-path}}$$

$$PE = \prod_{i=0}^N LE_i \cdot F_{oi} \cdot b_i$$

$$SE^* = \sqrt[N]{PE}$$

Example #2

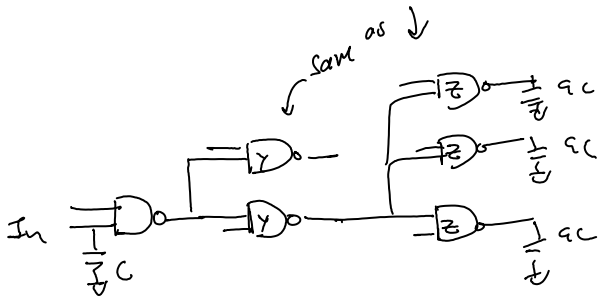

$$PE = \frac{4}{3} \cdot \frac{y}{C} \cdot \left(\frac{y+y}{y}\right) \cdot \frac{4}{3} \cdot \frac{z}{y} \left(\frac{z+z+z}{z}\right) \cdot \frac{4}{3} \cdot \frac{1}{z} \cdot 1$$

$$PE = 128 \quad SE^* = \sqrt[3]{128} = 5$$


$$\frac{4}{3} \cdot \frac{y}{C} \cdot 2 = 5 \Rightarrow y = \frac{15}{8} C$$

$$\frac{4}{3} \cdot \frac{z}{\frac{15}{8} C} \cdot 3 = 5 \Rightarrow z = \frac{5 \cdot 15}{32} \cdot C = \frac{75}{32} C$$

And now we have on sides.

$D = \text{plug} \& \text{chug}$

Practice Quiz

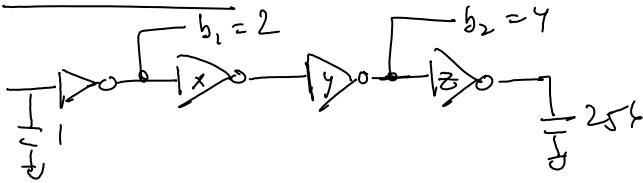

Find  $x, y, z$  to minimize delay

$$PE = \left(1 \cdot \frac{x}{1} \cdot 2\right) \cdot \left(1 \cdot \frac{y}{x}\right) \cdot \left(1 \cdot \frac{z}{y} \cdot 4\right) \cdot \left(1 \cdot \frac{256}{z}\right)$$

$$PE = 2 \cdot 4 \cdot 256 = 512 \cdot 4 = 1024 \cdot 2 = 2048$$

$$\Rightarrow SE^* = \sqrt[4]{2048} \approx 6.73$$

$$1 \cdot \frac{x}{1} \cdot 2 = 6.73 \Rightarrow x = 3.37$$

$$1 \cdot \frac{y}{3.37} = 6.73 \Rightarrow y = 22.68$$

$$1 \cdot \frac{z}{22.68} \cdot 4 = 6.73 \Rightarrow z = 38.16$$